

## I. DESIGN OF TYPE-I SECOND ORDER PLL

A type-I second order PLL is shown in Fig 1. The gain ( $K_{VCO}$ ) of the oscillator is 150 MHz/V with center frequency of 1 GHz. The gain of the phase detector ( $K_{PD}$ ) is  $\frac{2}{\pi}$  V/rad.

1. Design and Simulate a Type-I Second order PLL for the following cases:-

Case:I Design R and C for  $\zeta = 0.707$ .

Case:II Design R and C for  $\zeta = 1$ .

Case:III Design R and C for  $\zeta = 5$ .

where,

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}, \quad \omega_{LPF} = \frac{1}{RC}$$

In which of the above cases, PLL locks with the reference input faster?

2. Determine the settling time within 2% tolerance for the case I and verify from the simulations.
3. Observe the settling time and steady state phase error for the above three cases in the simulations.

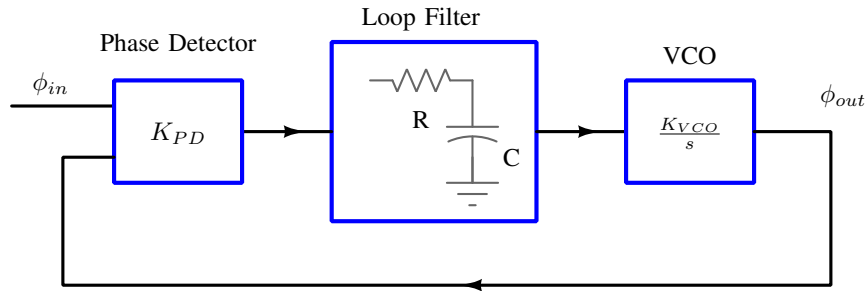


Fig. 1. Type I second order PLL

For PLL simulations using ideal blocks

- 1). You can use phase detector and VCO blocks from ahdLib in cadence virtuoso.
- 2). You should first simulate and verify the phase detector and VCO characteristics before keeping them in the feedback.
- 3). Use transient analysis to know  $K_{PD}$  of the phase detector.

Hints:-

1). The closed loop transfer of second order system is given as:

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad (1)$$

2). The closed loop transfer of second order PLL is given as:

$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{K_{PD}K_{VCO}}{RCs^2 + s + K_{PD}K_{VCO}} \quad (2)$$

3). Compare Eq. (1) and Eq. (2) ,

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}, \quad \omega_{LPF} = \frac{1}{RC}$$
$$\omega_n = \sqrt{K_{PD}K_{VCO}\omega_{LPF}}$$
 (3)

4). The settling time within 2% tolerance for  $0 < \zeta < 1$  is given by

$$T_s = \frac{4}{\zeta\omega_n} \quad (4)$$